

## Question Bank (I scheme)

**Name of Subject: Digital Techniques and Microprocessor (DTM)**  
**Subject code: 22323**  
**Semester: III**

**Unit Test: I**  
**Course: IF**

### CHAPTER-1 Number Systems, Digital Logic families and Logic Gates (16 Marks)

#### Marks 2

1. List the applications of digital system.(CO1)
2. Convert the following: - a)  $(420)_{10} = (?)_2$  (CO1)  
b)  $(10110)_2 = (?)_{10}$
3. Compare analog and digital signal.(CO1)
4. Define: - 1) Propagation delay 2) Noise margin 3) Fan in – fan out (CO1)
5. Perform the binary arithmetic.(CO1)
  - a)  $(11011.11)_2 + (11011.01)_2 = (?)_2$
  - b)  $(11101.1101)_2 - (101.011)_2 = (?)_2$
6. Convert a) 1110 gray to binary (CO1)  
b) 1011 binary to gray

#### Marks 4

1. Convert the following:- (CO1)
  - 1)  $(498.25)_{16} = (?)_{10}$
  - 2)  $(101100101)_2 = (?)_{16}$
  - 3)  $(B689D)_{16} = (?)_8$
  - 4)  $(110110111)_2 = (?)_{10}$
2. Perform BCD addition:- (CO1)
  - a)  $(435)_{10} + (129)_{10}$
  - b)  $(299)_{10} + (498)_{10}$
3. Subtract using 2's complement:- (CO1)
  - a)  $(11011)_2 - (1010)_2$
  - b)  $(10111)_2 - (11000)_2$
4. Compare between TTL and CMOS logic families.(CO1)
5. State any 6 Boolean laws. (CO1)
6. State and prove De Morgan's theorems.(CO1)
7. Draw symbol, truth table and logic equations of Ex-OR and EX-NOR gate(CO1)
8. Simplify the following and realize it using basic gates.(CO1)

a)  $Y = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} \overline{C} + A \overline{B} C + \overline{A} B \overline{C}$

b)  $Y = \overline{A} \overline{B} + \overline{A} \overline{B} + A \overline{B}$

## CHAPTER-2 Combinational Logic Circuits (Marks 14)

### Marks 2

1. Convert following expressions into canonical sop form(CO2)

a)  $\overline{A} + \overline{B} \overline{C} \overline{D}$

b)  $\overline{A} \overline{B} \overline{C} + \overline{B} \overline{D}$

2. Convert following expression into canonical pos form (CO2)

a)  $(A + \overline{B})(A + C)(B + \overline{C})$

b)  $(A + C)\overline{(A+B)}\overline{(A+C)}$

3. Design half adder using k-map and basic gates.(CO2)

4. Design half subtractor using k-map and basic gates.(CO2)

### Marks 4

1. Simplify the following using k-map and realize using NAND gates: .(CO2)

a)  $f(A,B,C,D) = \sum m(0,2,5,13,15)$

b)  $f(A,B,C,D) = \sum m(1,5,7,9,11,13,15)$

2. Simplify the following equation using k-map and realize it using logic gates: .(CO2)

a)  $Y = \sum m(0, 1, 2, 3, 8, 10) + \sum d(5, 7)$

b)  $Y = \sum m(0, 1, 4, 5) + \sum d(6, 7, 14, 15)$

3. Solve pos expression using k-map: .(CO2)

a)  $f(A, B, C) = \pi m(2, 3, 4, 5, 6, 7)$

b)  $f(A, B, C, D) = \pi m(1, 3, 5, 7, 8, 10, 14)$

4. Draw block diagram , truth table , logical expressions of logic diagram of 4:1 multiplexer. .(CO2)

5. Obtain an 8:1 Mux using 4:1 multiplexer. .(CO2)

6. Draw block diagram of 1:4 De-multiplexer and write down truth table. .(CO2)

## CHAPTER-3 Sequential Logic Circuits (Marks -12)

### Marks 2

1. Differentiate between combinational circuit and sequential circuit.(CO3)

2. Describe different types of triggering methods for a flip-flop.(CO3)

### Marks 4

3. Draw S-R latch using NAND gate only.(CO3)